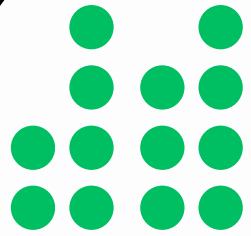


BCD-WRISTWATCH

A pcb wristwatch using a display of 13 led using binary coded decimal 1248.

Bangkok, Thailand

05/2026



Through hole resistor
because smd SUCKS!

shift register
74hc595


32.668khz
oscillating crystal

attiny85

tactile button

smd led
w/power indicator

charge via usb-c

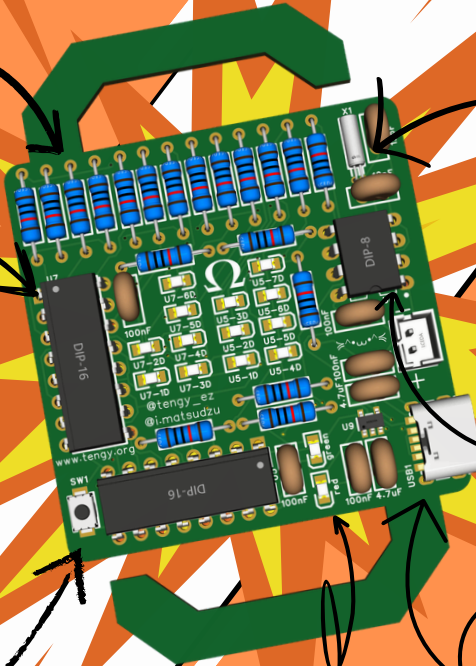

Make it!

The "kool" factor

- design with a hook to hot swap watch strap.
- use external lipo-battery for slim design.
- 22.75² mm board size perfect for wrist.
- only one button for setting time.
- use iconic green soldermask.

かっこいいから追加しました MADE BY TENG-KIM AGE: 15